

## Laboratory 1: Circuit Analysis Methods

Msc. Aerospace Engineering, Técnico, University of Lisbon

Circuit Theory and Electronics Fundamentals

March 25, 2021

### Contents

<b>1</b>	<b>Introduction</b>	<b>1</b>
<b>2</b>	<b>Theoretical Analysis</b>	<b>2</b>
2.1	Mesh Method . . . . .	3
2.2	Node Method . . . . .	3
2.3	Theoretical Analysis Results . . . . .	3
<b>3</b>	<b>Simulation Analysis</b>	<b>3</b>
3.1	Operating Point Analysis . . . . .	3
<b>4</b>	<b>Conclusion</b>	<b>4</b>

### 1 Introduction

The laboratory assignment presented has of its purpose the study of a circuit structured in four elementary meshes, through which exist seven resistors  $R_i$ , a voltage source  $V_a$ , a current controlled voltage source  $V_c$ , a current source  $I_d$  and a voltage controlled current source  $I_b$ . The circuit can be seen in Figure-1.

Lorem ipsum dolor sit amet, consectetur adipiscing elit. Ut purus elit, vestibulum ut, placerat ac, adipiscing vitae, felis. Curabitur dictum gravida mauris. Nam arcu libero, nonummy eget, consectetur id, vulputate a, magna. Donec vehicula augue eu neque. Pellentesque habitant morbi tristique senectus et netus et malesuada fames ac turpis egestas. Mauris ut leo. Cras viverra metus rhoncus sem. Nulla et lectus vestibulum urna fringilla ultrices. Phasellus eu tellus sit amet tortor gravida placerat. Integer sapien est, iaculis in, pretium quis, viverra ac, nunc. Praesent eget sem vel leo ultrices bibendum. Aenean faucibus. Morbi dolor nulla, malesuada eu, pulvinar at, mollis ac, nulla. Curabitur auctor semper nulla. Donec varius orci eget risus. Duis nibh mi, congue eu, accumsan eleifend, sagittis quis, diam. Duis eget orci sit amet orci dignissim rutrum.

Throughout the report it is presented a theoretical analysis, a simulation of the circuit and its analysis and a comparison of results.

In Section 2, the are applied both mesh and nods methods, to do a theoretical analysis of the circuit, using the Octave maths tool. In Section 3, it is executed an analysis of the circuit using the Ngspice tool to simulate it. Lastly, in Section 4, it is performed a comparison between the results from both the theoretical analysis and the simulation, from Section 2 and Section 3, respectively.

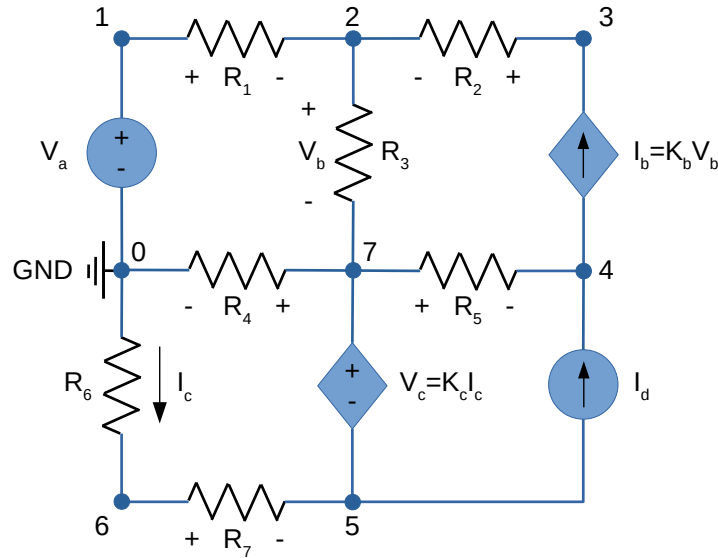


Figure 1: Circuit.

## 2 Theoretical Analysis

In this section, the circuit shown in Figure 1 is analysed theoretically. This analysis is based on circuit analysis basic principles, such as KVL (Kirchoff Voltage Law), KCL (Kirchoff Current Law) and Ohm's Law.

- **KVL:** This law states that the algebraic sum of all the voltages around any closed loop in a circuit is equal to zero. This means, that the sum of all the potential differences in a closed loop must be zero. This law is directly related with the Energy Conservation principle: if we circulate the loop in one direction, we will end up just where we have started. Therefore, there cannot be any potential difference between the start and the end node, since they are the same node and energy cannot be lost. Notice, that for this assumption to be true, polarities and signs of the elements must be taken in account:

$$\sum_{i=1}^n V_i = 0$$

- **KCL:** This law states that the algebraic sum of all the currents entering a node is equal to algebraic sum of all the currents leaving that same node. This law is also known as the Charge Conservation law: when a current enters a node it has no other option besides leaving the node, since that cannot be any current loss:

$$\sum_{i=1}^n I_i = 0$$

- **Ohm's Law:** Ohm's Law states that the current passing through a conductor is proportional to the voltage drop between the two terminals of that conductor:

$$V = RI,$$

where  $R$  represents the proportionality constant (resistance).

In order to analyse the circuit two different methods were used: (1) Mesh Method?? and (2) Node Method??.

## 2.1 Mesh Method

## 2.2 Node Method

## 2.3 Theoretical Analysis Results

Name	Value [A or V]
$I_b$	-2.263725e-04
$I_d$	1.011815e-03
$I_{R1}$	2.161226e-04
$I_{R2}$	-2.263725e-04
$I_{R3}$	-1.024993e-05
$I_{R4}$	1.194589e-03
$I_{R5}$	-1.238187e-03
$I_{R6}$	9.784660e-04
$I_{R7}$	9.784660e-04
$V_1$	5.125627
$V_2$	4.903891
$V_3$	4.446215
$V_4$	8.768409
$V_5$	-2.982745
$V_6$	-1.975719
$V_7$	4.934963

Table 1: Operating point. A variable preceded by @ is of type *current* and expressed in Ampere; other variables are of type *voltage* and expressed in Volt.

## 3 Simulation Analysis

### 3.1 Operating Point Analysis

Table 2 shows the simulated operating point results for the circuit under analysis.

Name	Value [A or V]
gib[i]	-2.26373e-04
id[current]	1.011815e-03
r1[i]	2.161226e-04
r2[i]	-2.26373e-04
r3[i]	-1.02499e-05
r4[i]	1.194589e-03
r5[i]	-1.23819e-03
r6[i]	9.784660e-04
r7[i]	9.784660e-04
v(1)	5.125627e+00
v(2)	4.903891e+00
v(3)	4.446215e+00
v(4)	8.768409e+00
v(5)	-2.98275e+00
v(6)	-1.97572e+00
v(7)	4.934963e+00
v(8)	-1.97572e+00

Table 2: Operating point. A variable followed by [i] or [current] is of type *current* and expressed in Ampere; other variables are of type *voltage* and expressed in Volt.

As we can see, the simulation results are similar to the ones we obtained in the section 2, concerning both the numerical values and the directions. Note that, unlike the table 1, in the simulation results we present an extra voltage at node 8,  $V_8$ , that is a "dummy" node used to compute the dependent voltage source.

## 4 Conclusion

After the theoretical analysis and the simulation, it can be concluded that the objective of the work, the study of the circuit presented in Figure-1, has been accomplished.

There were performed a theoretical analysis, applying both mesh and nodes methods, using the Octave maths tool, and a circuit simulation, using the Ngspice tool, with which it is clear a seamless match of the theoretical and the simulation results. The achievement of the equality in results comes from the components of the circuit, which are all linear and, therefore, both models have to present the same results.